

**ANALOG ,DIGITAL AND POWER ELECTRONICS 100 IMPORTANT MCQ**  
**NOTE-BOLD OPTION IS RIGHT ANSWER**

1. The p-region has a greater concentration of \_\_\_\_\_ as compared to the n-region in a P-N junction.  
A) **holes** B) electrons C) both holes & electrons D) phonons
2. A p-type semiconductor material is doped with \_\_\_\_\_ impurities whereas a n-type semiconductor material is doped with \_\_\_\_\_ impurities  
A) **acceptor, donor** B) acceptor, acceptor C) donor, donor D) donor, acceptor
3. In the p & n regions of the p-n junction the \_\_\_\_\_ & the \_\_\_\_\_ are the majority charge carriers respectively.  
A) holes, holes B) electrons, electrons C) **holes, electrons** D) electrons, holes
4. The n-region has a greater concentration of \_\_\_\_\_ as compared to the p-region in a P-N junction diode.  
A) holes B) **electrons** C) both holes & electrons D) phonons
5. Which of the below mentioned statements is false regarding a p-n junction diode?  
A) Diodes are uncontrolled devices B) Diodes are rectifying devices  
C) Diodes are unidirectional devices D) **Diodes have three terminals**
6. In the p & n regions of the p-n junction the \_\_\_\_\_ & the \_\_\_\_\_ are the minority charge carriers respectively.  
A) holes, holes B) electrons, electrons C) holes, electrons D) **electrons, holes**
7. Let's assume that the doping density in the p-region is  $10^{-9} \text{ cm}^{-3}$  & in the n-region is  $10^{17} \text{ cm}^{-3}$ , as such the p-n junction so formed would be termed as a  
A)  $p^- n^-$  B)  **$p^+ n^-$**  C)  $p^- n^+$  D)  $p^+ n^+$
8. When a physical contact between a p-region & n-region is established which of the following is most likely to take place?  
A) Electrons from N-region diffuse to P-region B) Holes from P-region diffuse to N-region  
C) **Both of the above mentioned statements are true** D) Nothing will happen
9. Which of the following is true in case of an unbiased p-n junction diode?  
A) Diffusion does not take place  
B) Diffusion of electrons & holes goes on infinitely  
C) There is zero electrical potential across the junctions  
D) **Charges establish an electric field across the junctions**

11. The arrow direction in diode symbol indicates
- A) Direction of electron flow **B) Direction of holes flow**
- C) Opposite to Direction of hole flow D) none of the above
12. When the diode is forward biased, it is equivalent to
- A) an off switch. B) **an on switch**. C) a high resistance. D) none of the above.
13. When transistors are used in digital circuits they usually operate in the:
- A) active region B) breakdown region C) **saturation and cutoff regions** D) linear region
14. A transistor has a  $\beta_{DC}$  of 250 and a base current,  $I_B$ , of 20  $\mu$  A. The collector current,  $I_C$ , equals:
- A. 500  $\mu$  A
- B. 5 mA**
- C. 50 mA
- D. 5 A
15. A current ratio of  $I_C/I_E$  is usually less than one and is called:
- A. beta B. theta
- C. **alpha** D. omega
16. The ends of a load line drawn on a family of curves determine:
- A. Saturation and cutoff**
- B. The operating point
- C. The power curve
- D. The amplification factor



B.  $I_C + I_E$

C.  $I_B + I_C$

D.  $I_B - I_C$

23. For a C-C configuration to operate properly, the collector-base junction should be reverse biased, while forward bias should be applied to which junction?

A. **collector-emitter**

B. base-emitter

C. collector-base

D. cathode-anode

24. What is the collector current for a C-E configuration with a beta of 100 and a base current of  $30 \mu\text{A}$ ?

A.  $30 \mu\text{A}$

B.  $.3 \mu\text{A}$

C. **3 mA**

D. 25. MA

25. The most commonly used transistor circuit arrangement is

A) Common base **B. common emitter.** C) common collector D) None of the above.

26. The input/output relationship of the common-collector and common-base amplifiers is:

A. 270 degrees

B. 180 degrees

C. 90 degrees

**D. 0 degrees**

27. With a PNP circuit, the most positive voltage is probably:

A. **ground**

B.  $V_C$

C.  $V_{BE}$

D.  $V_{CC}$

A.     0.05


B.     20

C.     **50**

D.     500

a) single pulse rectifier b) multiple pulse rectifier c) **two pulse rectifier** d) three pulse

38. The below shown circuit is that of a

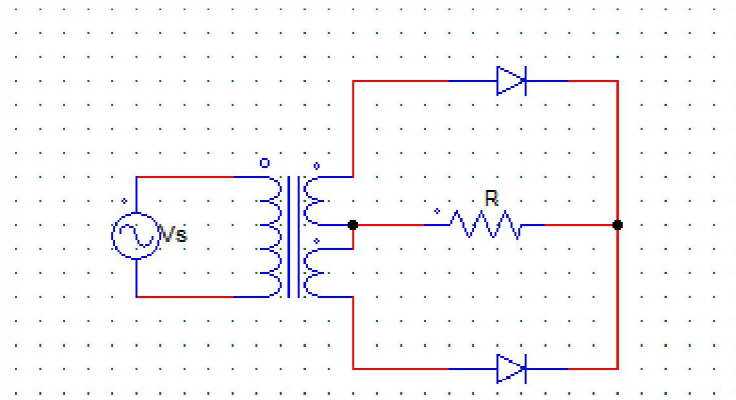


- a) full wave B-2 type connection **b) full wave M-2 type connection**  
 c) half wave B-2 type connection d) half wave M-2 type connection

39. In a 1-phase full wave bridge rectifier with M-2 type of connection has secondary side voltage  $V_s = V_m \sin \omega t$ , with R load & ideal diodes.

The expression for the average value of the output voltage can be given by

- a)  $2V_m/\pi$**  b)  $V_m/\pi$  c)  $V_m/\sqrt{2}$  d)  $2V_m/\sqrt{2}$

40. The below shown circuit is that of a

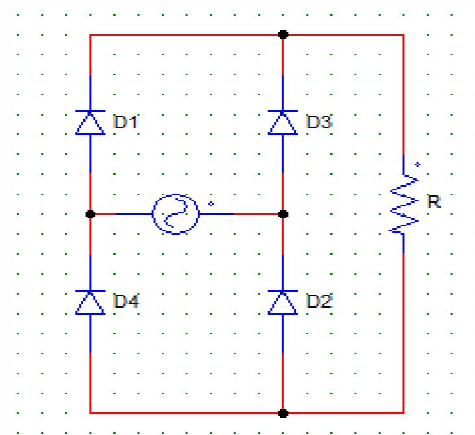


- a) full wave B-2 type connection** b) full wave M-2 type connection  
 c) half wave B-2 type connection d) half wave B-2 type connection

41. In a 1-phase full wave bridge rectifier with M-2 type of connection has secondary side voltage  $V_s = V_m \sin \omega t$ , with R load & ideal diodes.

The expression for the rms value of the output voltage can be given by

- a)  $V_m/\pi$  **b)  $V_m/\sqrt{2}$**  c)  $V_m$  d)  $V_m^2$

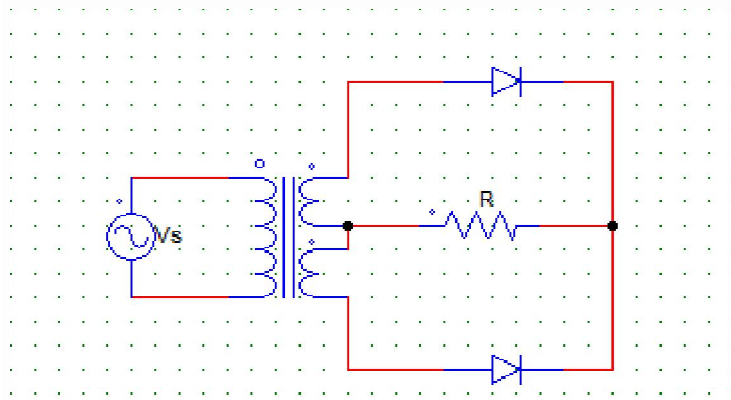42. For the circuit shown below, find the power delivered to the R load



Where,


$V_s = 230\text{V}$  AND  $V_s$  is the secondary side single winding rms voltage.  $R = 1\text{K}\Omega$

a) 46 W **b) 52.9 W** c) 67.2 W d) 69 W

43. The PIV experienced by the diodes in the mid-point type configuration is

a)  $V_m$  **b)  $2V_m$**  c)  $4V_m$  d)  $V_m/2$

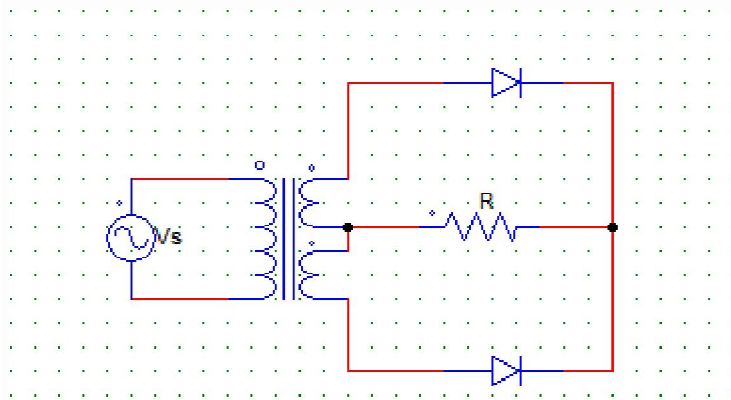44. For the circuit shown below, find the value of the average output current.



Where,  $V_s = 230\text{V}$  AND  $R = 1\text{K}\Omega$

$V_s$  is the secondary side single winding rms voltage.

a) 100mA b) 107mA c) 200mA **d) 207mA**

45. In the circuit, let  $I_m$  be the peak value of the sinusoidal source current. The average value of the diode current for the below given configuration is

(A) Figure A **(B) Figure B** (C) Figure C (D) None of the figures shown.

47. Which of the following equipment needs direct current?

(A) Relays B) Telephones (C) Time switches (D) **All of the above.**

48. In large motor generator sets ac motor is usually

(A) induction motor squirrel cage type **(B) synchronous motor**

(C) induction motor wound rotor type (D) any of the above.

49. The rms value of half wave-rectified sine wave with  $i_m$  as peak value is

(A)  $0.707 i_m$  (B)  $0.66 i_m$  **(C)  $0.5 i_m$**  (D)  $0.318 i_m$ .

50. Peak inverse voltage for a diode is the

(A) voltage corresponding to rated maximum voltage

(B) maximum voltage that can be applied across the diode in the conducting direction

**(C) maximum voltage that can be applied across the diode in the non-conducting direction**

(D) none of the above.

**Answers: 1. A 2. A 3. C 4.B 5.D 6.D 7.B 8.C 9.D 10.A 11.B 12.B 13.C 14.B 15.C**

**16.A 17.A 18.B 19.D 20.D 21.B 22.C 23.A 24.C 25.B 26.D 27.A 28.C 29.A 30.C 31.B 32.B 33.**

**B 34.B 35.B 36.B 37.C 38.B 39.A 40.A 41.B 42.B 43.B 44.D 45.B 46.C 47.D 48.B 49.C 50.C**



## ANALOG AND DIGITAL ELECTRONICS

1. In Active mode operation Transistor input & Output junctions respectively  
A) **Forward bias, Reverse bias** B) Reverse bias, Forward bias  
C) Forward bias, Forward bias D) Reverse bias, Reverse bias
2. In Cut-off mode operation Transistor input & Output junctions respectively  
A) Forward bias, Reverse bias B) Reverse bias, Forward bias  
C) Forward bias, Forward bias **D) Reverse bias, Reverse bias**
3. In Saturation mode operation Transistor input & Output junctions respectively  
A) Forward bias, Reverse bias B) Reverse bias, Forward bias  
**C) Forward bias, Forward bias** D) Reverse bias, Reverse bias
4. During Active mode Transistor becomes  
A) Rectifier **B) Amplifier** C) Clipper D) None of these
5. H-Parameters means  
A) Transmission B) Impedance **C) Hybrid** D) None of these
6. Transistor H-Parameters  
A)  **$h_{11}, h_{12}, h_{21}, h_{22}$**  B)  $h_{21}, h_{23}, h_{24}, h_{22}$  C)  $h_{23}, h_{22}, h_{25}, h_{26}$
7. In Hybrid Parameters  $h_{11}$  is called  
A) Forward current gain B) Reverse Voltage gain **C) Input Impedance** D) Output Admittance
8. In Hybrid Parameters  $h_{12}$  is called  
A) Forward current gain **B) Reverse Voltage gain** C) Input Impedance D) Output Admittance
9. In Hybrid Parameters  $h_{21}$  is called  
**A) Forward current gain** B) Reverse Voltage gain C) Input Impedance D) Output Admittance
10. In Hybrid Parameters  $h_{22}$  is called  
A) Forward current gain B) Reverse Voltage gain C) Input Impedance **D) Output Admittance**
11. With Positive Feed Back gain  
**A) Increases** B) Decreases C) Both D) None of these
12. With Negative Feed Back gain

A) Increases **B) Decreases** C) Both A&B D) None of these

13. With Negative Feed Back Stability

A) **Increases** B) Decreases C) Both A&B D) None of these

14. With Positive Feed Back Stability

A) Increases **B) Decreases** C) Both A&B D) None of these

15. With Positive Feed Back Bandwidth

A) Increases **B) Decreases** C) Both A&B D) None of these

16. With Negative Feed Back Bandwidth

**A) Increases** B) Decreases C) Both A&B D) None of these

17. With Positive Feed Back Noise & Distortion

A) Increases **B) Decreases** C) Both A&B D) None of these

18. With Negative Feed Back Noise & Distortion

**A) Increases** B) Decreases C) Both A&B D) None of these

19. Binary Number System is having Base of

A) 1 **B) 2** C) 3 D) 0

20. In Binary Number System the output states

**A) 0,1** B) 1,1 C) 0,0 D) 2,0



21. Which of the following is AND gate

**A)**

**B)**

**C)**

**D) None**

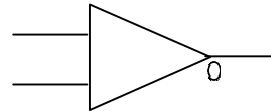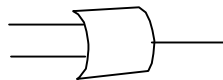




22. Which of the following is OR gate

**A)**

**B)**

**C)**

**D) None**

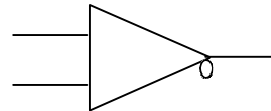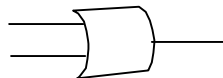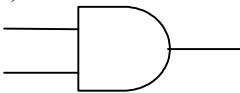



23. Which of the following is NOT gate

**A)**

**B)**

**C)**

**D) None**

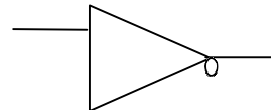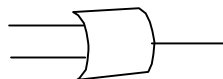




24. Which of the following is NOR gate

**A)**

**B)**


**C)**

**D) None**

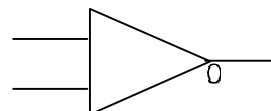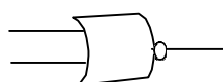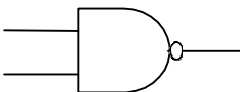


25. Which of the following is NAND gate


A)

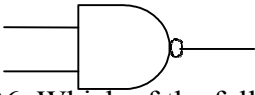

B)

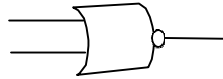


C)

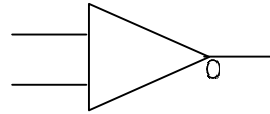


D) None

26. Which of the following is XOR gate


A)

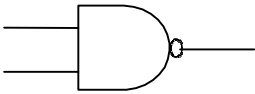

B)

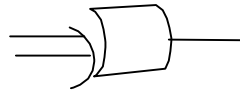


C)

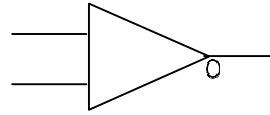

D) None

27. Which of the following is XNOR gate


A)

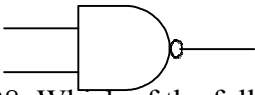

B)



C)

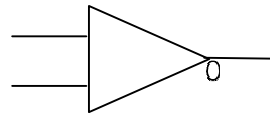

D) None

28. Which of the following is Universal Gate

A) NAND B) NOR C) Both A&B D) None of these

29. Expression for Two input AND Gate

A)  $AB$  B)  $A+B$  C)  $A-B$  D)  $A/B$

30. Expression for Two input OR Gate

A)  $AB$  B)  $A+B$  C)  $A-B$  D)  $A/B$

31. Expression for Two input NAND Gate

A)  $\overline{AB}$  B)  $\overline{A+B}$  C)  $A-B$  D)  $A/B$

32. Expression for Two input NOR Gate

A)  $\overline{AB}$  B)  $\overline{A+B}$  C)  $A-B$  D)  $A/B$

33. Expression for Two input XOR Gate

A)  $\overline{A}B + A\overline{B}$  B)  $\overline{A}B + AB$  C) Both D) None of these

34. Expression for Two input XNOR Gate

A)  $\overline{A}B + A\overline{B}$  B)  $\overline{A}B + AB$  C) Both D) None of these

35. According to Boolean Algebra  $A+0 =$

A)  $A$  B)  $0$  C)  $1$  D) None of these

36. According to Boolean Algebra  $A+1 =$

A)  $A$  B)  $0$  C)  $1$  D) None of these

37. According to Boolean Algebra  $A.0 =$

A) A B) 0 C) 1 D) None of these

38. According to Boolean Algebra  $A.1 =$

A) A B) 0 C) 1 D) None of these

39. According to Boolean Algebra  $A.A =$

A) A B) 0 C) 1 D) None of these

40. According to Boolean Algebra  $A+A =$

A) A B) 0 C) 1 D) None of these

41. According to Demorgan's theorem  $\overline{A+B+C+D} =$ -----

A)  $\overline{A}+\overline{B}+\overline{C}+\overline{D}$ ----- B)  $\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D}$ ----- C) Both A & B D) None of these

42. According to Demorgan's theorem  $\overline{A \cdot B \cdot C \cdot D} =$ -----

A)  $\overline{A}+\overline{B}+\overline{C}+\overline{D}$ ----- B)  $\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D}$ ----- C) Both A & B D) None of these

43. In Any Flip Flop No. of States

A) 2 B) 1 C) 0 D) None of these

44. SR Flip Flop is called

A) SET-RESET B) RESET-SET C) Both A & B D) None of these

45. In D-Flip Flop Output is

A) Same as Input B) 0 C) 1 D) None of these

46. In OFF State output is

A) 1 B) 0 C) both A & B D) None of these

47. In ON State output is

A) 1 B) 0 C) both A & B D) None of these

48. In NOT Gate Output is

A) Complement of input B) Same of input C) both A & B D) None of these

49. In Which of the following Flip Flops Output Follows Input

A) J-K Flip Flop B) S-R Flip Flop C) D-Flip Flop D) None of these

50. The Expression for XOR Gate is

A)  $A+B$  B)  $AB$  C)  $A \oplus B$  D) None of these

**ANSWERS:** 1.A 2.D 3.C 4.B 5.C 6.A 7.C 8.B 9.A 10.D 11.A 12.B 13.A

14.B 15.B 16.A 17.B 18.A 19.B 20.A 21.A 22.B 23.C 24.B 25.A 26.B 27.B 28.C

29.A 30.B 31.A 32.B 33.B 34.A 35.A 36.C 37.B 38.A 39.A 40.A 41.B 42.A 43.A 44.A

45.A 46.B 47.A 48.A 49.C 50.D